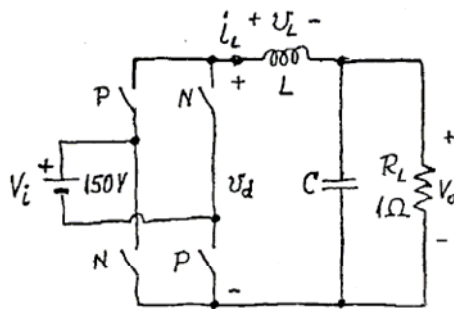
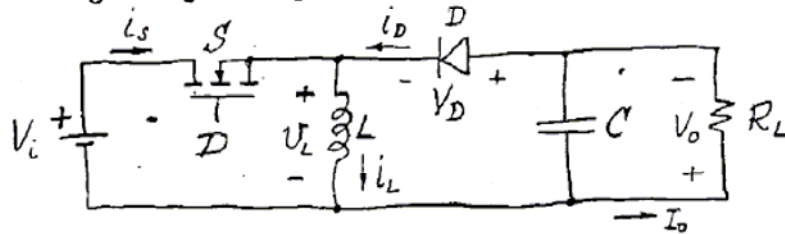


PROBLEM 1: Assume that all the components of the converter in Fig. 1 are ideal and that the capacitor C is very large. If the switches P and N are operated complementarily with constant switching frequency of 5 kHz and the duty cycle of the P switches is $D_P = 2/3$:

- Sketch the steady-state waveforms of v_d , v_L , and i_L , over one switching cycle.
- Find the output voltage V_o .
- Find the value of the inductance L so that the inductor current peak-to-peak ripple is $\Delta i_L \leq 10$ A.



PROBLEM 2: Dc-dc converter in Fig. 2 operates with $D = 1/3$ and delivers 450 W to the load of $R_L = 0.5 \Omega$. Find the efficiency of the converter if the diode forward voltage drop is $V_D = 1 \text{ V}$, MOSFET on-resistance is $R_{ON} \approx 100 \text{ m}\Omega$, while the switching losses and losses in C and L can be neglected. Assume that L and C are large enough to neglect influence of any current and voltage ripple.



PROBLEM 3: DC-DC converter in Fig. 3 operates in continuous current conduction mode with constant switching frequency. Assume that all the components are ideal and that L and C are large.

- Find the value of the switch duty cycle, D , so that $V_o = 15\text{ V}$ when $V_i = 12\text{ V}$.
- Sketch the steady-state waveforms of v_s , i_s , v_D , and i_D , over one switching cycle.
- Find the maximum voltage across the switch, S , and the switch average current.
- Find the maximum reverse voltage across the diode, D , and the diode average current.

